

Lab experiment: Part-1 RC circuits frequency response

1. Try to finish this part in the first hour.
2. Connect the RC circuit shown in Fig.1. Note: $R=1K\Omega$ and $C=1\mu F$
3. Observe input and output voltage waveforms for $V_{in} = 10V_{pp}$, $50Hz$ sinusoidal signal, $R=1K\Omega$ and $C=1\mu F$.

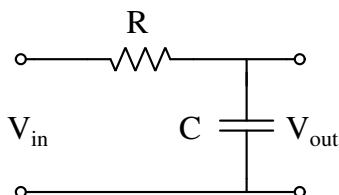


Figure 1: RC circuit

4. Vary the frequency of V_{in} from $50Hz$ to $50kHz$ with appropriate steps and measure V_{out} and phase difference between V_{out} and V_{in} keeping the magnitude of V_{in} constant.
5. Plot the frequency response (log magnitude and phase w.r.t. log frequency).
6. Explain your observations in the report.