

# EE236: Experiment 4 - Heart Rate Monitor

Mohd Safwan, 17D070047

August 18, 2018

## 1 Aim of the experiment

To make a heart rate monitor on the principle of PPG(photoplethysmogram) using TRCT5000 LED-phototransistor pair and then conditioning the output using op-amps.


## 2 Methods

Use TCRT5000, to record the output of PPG. Limit the sensor input using a resistor. Design a band pass filter using an opamp as a high pass filter and a second opamp as a low pass filter and finally amplify the signal and take the output on a DSO. Measure the time of pulse using cursors on DSO.

## 3 Results
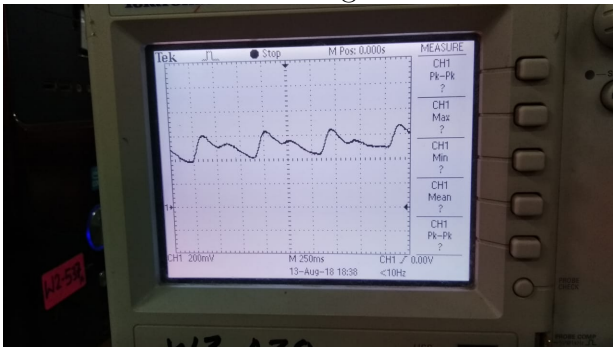
### 3.1 Observations

We can see that the difference between 2 consecutive systolic nodes is 14 divisions, where 1 division is  $250/5 = 50ms$ . Hence my heart-rate was  $60 * 1000 / (14 * 50) = 85.7$  bpm which is consistent with me being nervous at the time.



### 3.2 Inference

The output of the DSO shows a clean wave with systolic and diastolic peaks and dicrotic notches. The measured heart rate on the DSO matched the heart rate measured using pulses on the wrist.

## 4 Learning objectives

To combine various devices and to and how such a simple electronic circuits can help us in our day to day life.

## 5 Quick feedback

### 5.1 What about this experiment did you find helpful?

The fact that we learned to use TCRT5000 and to implement it in a circuit.

### 5.2 What about this experiment is still unclear?

The internal working of TCRT5000.

